



This quiz is worth a total of **100 points**.

In accordance with the Georgia Institute of Technology Honor Code, I have neither given nor received aid on this quiz.

Signature: _____

Please make sure all of your answers are contained within the answer boxes or the fill-in lines. Do not write your work in the answer boxes. You have been provided with extra paper for your scratch work. You will **NOT** be given credit for showing work. Having anything except the answer inside the boxes or above the fill-in lines reduces autograder performance and might cause incorrect results. **Make sure to write your name, username, and answers legibly. You will not receive credit for illegible answers.**

Digital Logic: Truth Table from Expression

- Complete the empty entries in the truth table with respect to the following boolean expression.

$$S = (A \& B) \mid C$$


A	B	C	S
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

16

Digital Logic: Truth Table from Circuit

- Complete the empty entries in the following truth table with respect to the circuit shown below.

Note: The 0 indicates a zero constant.

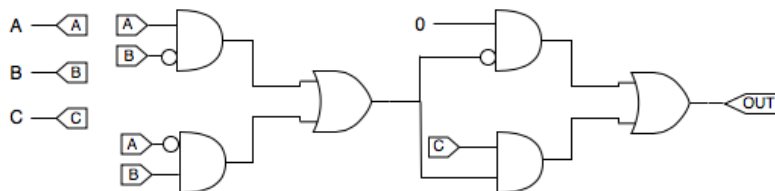

A	B	C	OUT
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

16

Short Answer

- For the following questions please answer in the space provided.

(a) Given a multiplexer with n select bits, what's the maximum number of outputs? _____

1

5

(b) Given a decoder with n select bits, what's the maximum number of outputs? _____

2^n

5

(c) Find an expression equivalent to $(\neg A \& \neg B)$ with ≤ 2 bitwise operators ($\neg, \&, \mid$) _____

$\neg(A \mid B)$

5

Multiple Choice

- For the following questions please fill-in the appropriate circle.

(a) Which operator should one use to set bits? ☐ AND ☒ OR ☐ XOR ☐ ADD

4

(b) Which operator should one use to clear bits? ☒ AND ☐ OR ☐ XOR ☐ ADD

4

(c) Which operator should one use to toggle bits? ☐ AND ☐ OR ☒ XOR ☐ ADD

4






Digital Logic: Adding and Subtracting

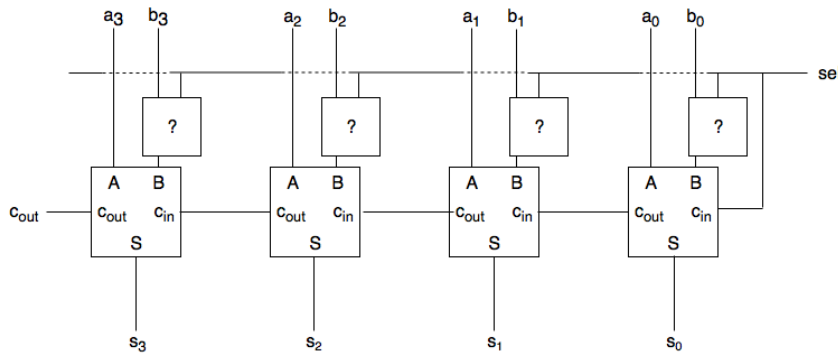5. Consider the following diagram of a 4-bit adder-subtractor composed of four 1-bit full-adders. When the **sel** input is 0 the circuit should compute the operation $A + B$. When the **sel** input is 1 the circuit should compute the operation $A - B$.

10

Hint: The **sel** input is connected both to the marked components and to the c_{in} of the first adder.



Which component should be inserted for the boxes with ?'s: ☐ AND ☐ OR ☒ XOR ☐ ADD

Bitmasking

6. Write a function which extracts all bits greater than and including the bit **i** from a 32-bit 2's complement integer such that:

16

- **num** is a 32-bit 2's complement integer
- **i** is the index bit with a range of (0, 31)

This must be completed in one line without multiplication, addition, division or modulus. All right shifts must be signed. **You may use subtraction!**

Note: Make sure your answer is of the form “**return ... ;**”

For example, `upperBits(0x98765432, 28) => 0x00000009`

```
public static int upperBits(int num, int i)
{
    return ((num >> i) & ~(~0x0 << (32 - i)));
}
```

Digital Logic: Circuit from Expression

7. Consider the following boolean expression with three inputs and one output: $Z = \overline{\overline{A} \mid (B \& \overline{C})}$.

15

Draw the corresponding circuit. **You are allowed (but not required) to simplify the expression!**

You may use any of the following symbols: NOT (\neg) AND (\sqcap) OR (\sqcup) XOR (\oplus).

Warning: If we cannot distinguish between your gates, you will receive NO credit.

A

B

Z

C

